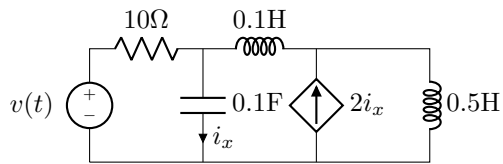


Lecture 32, Apr 1, 2022

Nodal and Mesh Analysis for AC Circuits




- $v(t) = 20 \cos(4t) \implies \mathbf{V} = 20 \angle 0^\circ$

* Impedances:

- $\mathbf{Z}_R = 10\Omega$
- $\mathbf{Z}_C = -\frac{j}{\omega C} = -\frac{j}{4 \cdot 0.1\text{F}} = -j2.5\Omega$
- $\mathbf{Z}_{L1} = j\omega L_1 = j4 \cdot 0.1 = j0.4\Omega$
- $\mathbf{Z}_{L2} = j\omega L_2 = j2\Omega$

* In the phasor domain:

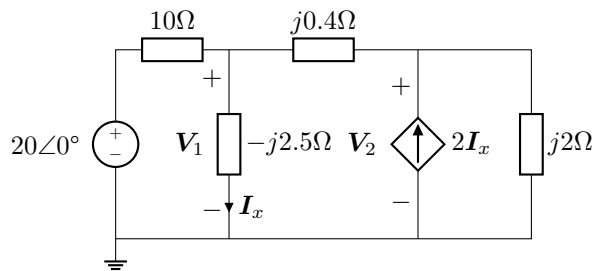

* $\mathbf{I}_x = \frac{\mathbf{V}_1}{\mathbf{Z}_C}$

* $\frac{\mathbf{V}_1 - 20}{\mathbf{Z}_R} + \frac{\mathbf{V}_1}{\mathbf{Z}_C} + \frac{\mathbf{V}_1 - \mathbf{V}_2}{\mathbf{Z}_{L1}} = 0$

* $\frac{\mathbf{V}_2 - \mathbf{V}_1}{\mathbf{Z}_{L1}} + \frac{\mathbf{V}_2}{\mathbf{Z}_{L2}} - 2\frac{\mathbf{V}_1}{\mathbf{Z}_C}$

* Solve the system as normal, then use nodal voltages to find phasor for $\mathbf{I}_x = \frac{\mathbf{V}_1}{\mathbf{Z}_C}$, and convert to time domain